

**ISTANBUL TECHNICAL UNIVERSITY**  
**COMPUTER ENGINEERING DEPARTMENT**

**BLG 222E**  
**COMPUTER ORGANIZATION**  
**PROJECT REPORT**

**PROJECT NO** : 3  
**PROJECT DATE** : 03.06.2020  
**GROUP NO** : G22

**GROUP MEMBERS:**

150180903 : Khayal HUSEYNOV  
150180901 : Ramal SEYIDLI  
150180725 : İsmayil Buğra KÜTÜKOĞLU  
150180720 : Kerim GENÇ

# Contents

## FRONT COVER

## CONTENTS

<b>1</b>	<b>INTRODUCTION</b>	<b>1</b>
<b>2</b>	<b>PROJECT LOGIC</b>	<b>3</b>
2.1	FETCH . . . . .	3
2.2	DECODE . . . . .	3
2.2.1	LD . . . . .	3
2.2.2	ST . . . . .	4
2.2.3	MOV . . . . .	4
2.2.4	PSH . . . . .	5
2.2.5	PUL . . . . .	6
2.2.6	ADD . . . . .	6
2.2.7	SUB . . . . .	8
2.2.8	DEC . . . . .	9
2.2.9	INC . . . . .	11
2.2.10	AND . . . . .	14
2.2.11	OR . . . . .	15
2.2.12	NOT . . . . .	16
2.2.13	LSL . . . . .	17
2.2.14	LSR . . . . .	18
2.2.15	BRA . . . . .	19
2.2.16	BEQ . . . . .	19
2.2.17	BNE . . . . .	19
2.2.18	CALL . . . . .	20
2.2.19	RET . . . . .	20
<b>3</b>	<b>PROJECT EQUATIONS</b>	<b>21</b>
3.1	ORIGINAL . . . . .	21
3.1.1	OutASel . . . . .	21
3.1.2	OutBSel . . . . .	21
3.1.3	RegSelRF . . . . .	22
3.1.4	FunSelRF . . . . .	22
3.1.5	MuxCSel . . . . .	23

3.1.6	FunSelALU . . . . .	23
3.1.7	MuxASel . . . . .	24
3.1.8	En . . . . .	25
3.1.9	L/H . . . . .	25
3.1.10	FunSelIR . . . . .	25
3.1.11	MuxBSel . . . . .	26
3.1.12	Store . . . . .	26
3.1.13	Load . . . . .	26
3.1.14	FunSelARF . . . . .	27
3.1.15	RegSelARF . . . . .	28
3.1.16	OutCSel . . . . .	28
3.1.17	OutDSel . . . . .	29
3.1.18	SC Clear . . . . .	29
3.2	COMPLETE . . . . .	30
3.2.1	RegSelRF . . . . .	30
3.2.2	FunSelRF . . . . .	31
3.2.3	OutBSel . . . . .	31
3.2.4	FunSelALU . . . . .	31
3.2.5	MuxASel . . . . .	32
3.2.6	FunSelARF . . . . .	32
3.2.7	OutCSel . . . . .	33
3.2.8	RegSelARF . . . . .	33
3.2.9	MuxBSel . . . . .	33
3.2.10	MuxCSel . . . . .	34
<b>4</b>	<b>RESULTS</b>	<b>34</b>
<b>5</b>	<b>DISCUSSION</b>	<b>35</b>
<b>6</b>	<b>CONCLUSION</b>	<b>35</b>

In project 3, we designed a Basic Computer and it is look like shown below. We made operations possible by using project 2. While we have designed Basic Computer in project 2 indeed, we updated it to control unit in this project.

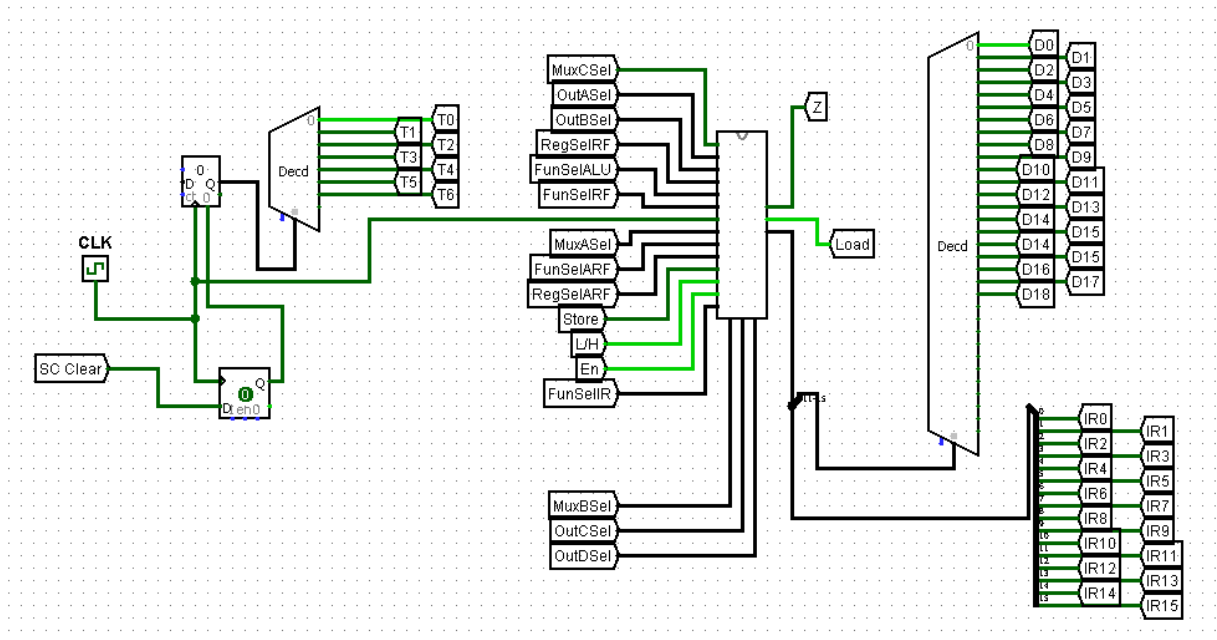


Figure 1: Main Circuit

We made it possible by applying instructions of opcode below:

OPCODE (HEX)	SYMB	ADDRESSING MODE	DESCRIPTION
0x00	LD	IM, D	$R_x \leftarrow \text{Value}$ (Value is described in Table 3)
0x01	ST	D	$\text{Value} \leftarrow R_x$
0x02	MOV	N/A	$\text{DESTREG} \leftarrow \text{SRCREG1}$
0x03	PSH	N/A	$M[\text{SP}] \leftarrow R_x, \text{SP} \leftarrow \text{SP} - 1$
0x04	PUL	N/A	$\text{SP} \leftarrow \text{SP} + 1, R_x \leftarrow M[\text{SP}]$
0x05	ADD	N/A	$\text{DESTREG} \leftarrow \text{SRCREG1} + \text{SRCREG2}$
0x06	SUB	N/A	$\text{DESTREG} \leftarrow \text{SRCREG2} - \text{SRCREG1}$
0x07	DEC	N/A	$\text{DESTREG} \leftarrow \text{SRCREG1} - 1$
0x08	INC	N/A	$\text{DESTREG} \leftarrow \text{SRCREG1} + 1$
0x09	AND	N/A	$\text{DESTREG} \leftarrow \text{SRCREG1} \text{ AND } \text{SRCREG2}$
0x0A	OR	N/A	$\text{DESTREG} \leftarrow \text{SRCREG1} \text{ OR } \text{SRCREG2}$
0x0B	NOT	N/A	$\text{DESTREG} \leftarrow \text{NOT SRCREG1}$
0x0C	LSL	N/A	$\text{DESTREG} \leftarrow \text{LSL SRCREG1}$
0x0D	LSR	N/A	$\text{DESTREG} \leftarrow \text{LSR SRCREG1}$
0x0E	BRA	IM	$\text{PC} \leftarrow \text{Value}$
0x0F	BEQ	IM	IF Z=1 THEN $\text{PC} \leftarrow \text{Value}$
0x10	BNE	IM	IF Z=0 THEN $\text{PC} \leftarrow \text{Value}$
0x11	CALL	IM	$M[\text{SP}] \leftarrow \text{PC}, \text{SP} \leftarrow \text{SP} - 1, \text{PC} \leftarrow \text{Value}$
0x12	RET	N/A	$\text{SP} \leftarrow \text{SP} + 1, \text{PC} \leftarrow M[\text{SP}]$

Figure 2: Opcode

 


Figure 3: Full Circuit

## 2 PROJECT LOGIC

RF refers to General Purpose Register File

ARF refers to Address Register File

### 2.1 FETCH

T0:  $IR(8-15) \leftarrow M[PC]$

OutDSel: 00; Select PC

Load: 1; Load  $M[PC]$

L/H: 1; Select  $IR(8-15)$

FunSelIR: 11; Load to chosen part of IR

En: 1;

T1:  $PC \leftarrow PC + 1$

RegSelARF: 001; Only enable PC

FunSelARF: 10; Increment registers

OutDSel: 00; Select PC

En: 0; Disable IR

T2:  $IR(0-7) \leftarrow M[PC]$

OutDSel: 00; Select PC

Load: 1; Load  $M[PC]$

L/H: 0; Select  $IR(0-7)$

FunSelIR: 11; Load to chosen part of IR

En: 1;

T3:  $PC \leftarrow PC + 1$

RegSelARF: 001; Only enable PC

FunSelARF: 10; Increment registers

OutDSel: 00; Select PC

En: 0; Disable IR

### 2.2 DECODE

#### 2.2.1 LD

D0:  $R_x \leftarrow \text{Value } IR(8) = 0$ , Addressing Mode is Immediate,

D0T4:

MuxASel: 00; Send IR(0-7) to RF

RegSelRF: decode(IR10,IR9); Enable given registers

FunSelRF: 01; Load to given registers

IR(8) = 1, Addressing Mode is Direct,

D0T4:

MuxBSel: 01; Send IR(0-7) to ARF

RegSelARF: 010; enable AR

FunSelARF: 01; Load to given registers

D0T5:

OutDSel: 01; Select AR

Load: 1; Load M[AR]

MuxASel: 01; Send M[AR] to RF

RegSelRF: decode(IR10,IR9); Enable given registers

FunSelRF: 01; Load to enabled registers

### **2.2.2 ST**

D1: Value  $\leftarrow$  Rx

Addressing Mode is Direct

So, D1: M[AR]  $\leftarrow$  Rx

D1T4:

MuxBSel: 01; Send IR(0-7) to ARF

RegSelARF: 010; Enable AR

FunSelARF: 01; Load to chosen registers

D1T5:

OutDSel: 01; Select AR

OutASel: IR10, IR9; Select Rx

MuxCSel: 1 Select A input of ALU as Rx

FunSelALU: 0000; Select A (Rx) as output of ALU

Store: 1; Store Rx to M[AR]

### **2.2.3 MOV**

D2: DESTREG  $\leftarrow$  SRCREG1

D2T4: IR10'IR7':  $RF \leftarrow RF$   
 OutASel: (IR6,IR5); Select SRCREG1  
 FunSelALU: 0000; Select A (SRCREG1) as output of ALU  
 MuxASel: 11; Choose the SRCREG1  
 RegSelRF: decode(IR9,IR8); Enable the desired DESTREG  
 FunSelRF: 01; Load to DESTREG

D2T4: IR10'IR7:  $RF \leftarrow ARF$   
 OutCSel: (IR6,IR5); Select SRCREG1  
 MuxASel: 10; Choose OutCSel as RF input  
 RegSelRF: decode(IR9,IR8); Enable the desired DESTREG  
 FunSelRF: 01; Load to DESTREG

D2T4: IR10IR7':  $ARF \leftarrow RF$   
 OutASel: (IR6,IR5); Select SRCREG1  
 MuxCSel: 1; Choose OutASel output as A input of ALU  
 FunSelALU: 0000; Select A (SRCREG1) as output of ALU  
 MuxBSel: 11; Select RF as input of ARF  
 RegSelARF: decode(IR9,IR8); Enable DESTREG  
 FunSelARF: 01 Load to DESTREG

D2T4: IR10IR7:  $ARF \leftarrow ARF$   
 OutCSel: (IR6,IR5); Select SRCREG1  
 MuxASel: 10; Select SRCREG1 as I0 of MuxC  
 MuxCSel: 0; Select SRCREG1 as input A of ALU  
 FunSelALU: 0000; Select SRCREG1 as output A of ALU  
 MuxBSel: 11; Select SRCREG1 as input of ARF  
 RegSelARF: decode(IR9,IR8); Enable DESTREG  
 FunSelARF: 01; Load to DESTREG

#### **2.2.4 PSH**

D3:  $M[SP] \leftarrow Rx, SP \leftarrow SP - 1$

D3T4:  $M[SP] \leftarrow RF$   
 OutASel: (IR10,IR9); Select REGSEL  
 MuxCSel: 1; Send REGSEL as input A of ALU  
 FunSelALU: 0000; Send REGSEL as output of ALU



OutDSel: 10; Send SP as Address to M  
Store: 1; Store REGSEL to M[SP]

D3T5:

RegSelARF: 100; Enable SP

FunSelARF: 11; Decrement SP

### **2.2.5 PUL**

D4:  $SP \leftarrow SP + 1$ ,  $Rx \leftarrow M[SP]$

D4T4:

RegSelARF: 100; Enable SP

FunSelARF: 10; Increment SP

D4T5:

OutDSel: 10; Select SP as Address to M

Load: 1; Write M

MuxASel: 01; Send M[SP] to input of RF

RegSelRF: decode(IR10,IR9); Enable REGSEL

FunSelRF: 01; Load M[SP] to REGSEL

### **2.2.6 ADD**

D5:  $DESTREG \leftarrow SRCREG1 + SRCREG2$

D5T4: IR10'IR7'IR4':  $RF \leftarrow RF + RF$

OutASel: (IR6,IR5); Select SRCREG1

MuxCSel: 1; Send SRCREG1 as input A of ALU

OutBSel: (IR3,IR2); Send SRCREG2 as input B of ALU

FunSelALU: 0100; Do the operation  $A + B$

MuxASel: 11; Send ALU output to RF input

RegSelRF: decode(IR9,IR8); Enable DESTREG

FunSelRF: 01; Load result to DESTREG

D5T4: IR10'IR7'IR4:  $RF \leftarrow RF + ARF$

LEFT FOR LATER (NEED PSH/PUL)

D5T4: IR10'IR7'IR4':  $RF \leftarrow ARF + RF$

LEFT FOR LATER (NEED PSH/PUL)

D5T4: IR10'IR7IR4:  $RF \leftarrow ARF + ARF$

REDUNDANT

D5T4: IR10IR7'IR4':  $ARF \leftarrow RF + RF$

OutASel: (IR6,IR5); Send SRCREG1 to MuxC

MuxCSel: 1; Send SRCREG1 to ALU

OutBSel: (IR3,IR2) Select SRCREG2

FunSelALU: 0100; Do the operation  $A + B$

MuxBSel: 11; Send ALU output to ARF input

RegSelARF: decode(IR9,IR8); Enable DESTREG

FunSelARF: 01; Load result to DESTREG

D5T4: IR10IR7'IR4:  $ARF \leftarrow RF + ARF$

OutCSel: (IR3,IR2); Send SRCREG2 to MuxA

MuxASel: 10; Send SRCREG2 to MuxC

MuxCSel: 0; Send SRCREG2 as input A of ALU

OutBSel: (IR6,IR5); send SRCREG1 as input B of ALU

FunSelALU: 0100; Do the operation  $A + B$

MuxBSel: 11; Send ALU output to ARF input

RegSelARF: decode(IR9,IR8); Enable DESTREG

FunSelARF: 01; Load result to DESTREG

D5T4: IR10IR7IR4':  $ARF \leftarrow ARF + RF$

OutCSel: (IR6,IR5); Send SRCREG1 to MuxA

MuxASel: 10; Send SRCREG1 to MuxC

MuxCSel: 0; Send SRCREG1 to A input of ALU

OutBSel: (IR3,IR2); Send SRCREG2 to B input of ALU

FunSelALU: 0100; Do the operation  $A + B$

MuxBSel: 11; Send ALU output to ARF input

RegSelARF: decode(IR9,IR8); Enable DESTREG

FunSelARF: 01; Load result to DESTREG

D5T4: IR10IR7IR4:  $ARF \leftarrow ARF + ARF$

REDUNDANT

### 2.2.7 SUB

D6: DESTREG  $\leftarrow$  SRCREG2 - SRCREG1

D6T4: IR10'IR4'IR7': RF  $\leftarrow$  RF - RF

OutASel: (IR3,IR2); Send SRCREG2 to MuxC

MuxCSel: 1; Send SRCREG2 as input A of ALU

OutBSel: (IR6,IR5); Send SRCREG1 as input B of ALU

FunSelALU: 0110; Do the operation A - B

MuxASel: 11; Send output of ALU to RF input

RegSelRF: decode(IR9,IR8); Enable DESTREG

FunSelRF: 01; Load result to DESTREG

D6T4: IR10'IR4'IR7: RF  $\leftarrow$  RF - ARF

REDUNDANT

D6T4: IR10'IR4IR7': RF  $\leftarrow$  ARF - RF

OutBSel: (IR6,IR5); Select SRCREG1 as B input of ALU

OutCSel: (IR3,IR2); Send SRCREG2 to MuxA

MuxASel: 10; Send SRCREG2 to MuxC

MuxCSel: 0; Select SRCREG1 as A input of ALU

D6T5:

FunSelALU: 0110; Do the operation A - B

MuxASel: 11; Send ALU output to RF input

RegSelRF: decode(IR9,IR8); enable DESTREG

FunSelRF: 01; Load result to DESTREG

D6T4: IR10'IR4IR7: RF  $\leftarrow$  ARF - ARF

REDUNDANT

D6T4: IR10IR4'IR7': ARF  $\leftarrow$  RF - RF

OutASel: (IR3,IR2); Send SRCREG2 to MuxC

MuxCSel: 1; Select SRCREG2 as A input of ALU

OutBSel: (IR6,IR5); Send SRCREG1 as B input of ALU

FunSelALU; 0110; Do the operation A - B

MuxBSel; 11; Send outALU to ARF input

RegSelARF: decode(IR9,IR8); Enable DESTREG

FunSelARF: 01; Load result to DESTREG

D6T4: IR10IR4'IR7:  $ARF \leftarrow RF - ARF$

REDUNDANT

D6T4: IR10IR4IR7':  $ARF \leftarrow ARF - RF$

OutCSel: (IR3,IR2); Select SRCREG2 to MuxA

MuxASel: 10; Send SRCREG 2 to MuxC

MuxCSel: 0; Send SRCREG as A input of ALU

OutBSel: (IR6,IR5); Send SRCREG1 as B input of ALU

FunSelALU: 0110; Do the operation A - B

MuxBSel: 11; Send outALU to ARF input

RegSelARF: decode(IR9,IR8); Enable DESTREG

FunSelARF: 01; Load result to DESTREG

D6T4: IR10IR4IR7:  $ARF \leftarrow ARF - ARF$

REDUNDANT

### 2.2.8 DEC

$DESTREG \leftarrow SRCREG1 - 1$

D7T4: IR10'IR7': IR9IR8 = IR6IR5:  $RF \leftarrow RF - 1$

RegSelRF: decode(IR6,IR5); Enable SRCREG1

FunSelRF: 11; Decrement SRCREG1 by 1

D7T5: Fixing flag

OutBSel: (IR6,IR5); Send SRCREG1 to B input of ALU

FunSelALU: 0001; Send B as outALU

D7T4: IR10'IR7': IR9IR8 != IR6IR5:  $RF \leftarrow RF - 1$

RegSelRF: decode(IR6,IR5); Enable SRCREG1

FunSelRF: 11; Decrement SRCREG1 by 1

D7T5:

OutBSel: (IR6,IR5); Send SRCREG1 (decremented) to B input of ALU

FunSelALU: 0001; Print outALU as SRCREG1 (decremented)

MuxASel: 11; Send outALU to RF input

RegSelRF: decode(IR9,IR8); Enable DESTREG  
 FunSelRF: 01; Load result to DESTREG  
 D7T6:  
 OutBSel: (IR9,IR8); Send DESTREG to ALU B input  
 FunSelALU: 0001; Print outALU as SRCREG1  
 RegSelRF: decode(IR6,IR5); Enable SRCREG1  
 FunSelRF: 10; Increment SRCREG1 back to its original value

D7T4: IR10'IR7:  $RF \leftarrow ARF - 1$   
 RegSelARF: decode(IR6,IR5); Enable SRCREG1  
 FunSelARF: 11; Decrement SRCREG1 by 1

D7T5:  
 OutCSel: (IR6,IR5); Send SRCREG1 (decremented) to MuxA  
 MuxASel: 10; Send SRCREG1 to RF input  
 RegSelRF: decode(IR9,IR8); Enable DESTREG  
 FunSelRF: 01; Load to DESTREG

D7T6:  
 OutBSel: (IR9,IR8); Send DESTREG to B input of ALU  
 FunSelALU: 0001; Print outALU as DESTREG  
 RegSelARF: decode(IR6,IR5); Enable SRCREG1  
 FunSelARF: 10; Increment SRCREG1 back to its original value

D7T4: IR10IR7':  $ARF \leftarrow RF - 1$   
 RegSelRF: decode(IR6,IR5); Enable SRCREG1  
 FunSelRF: 11; Decrement SRCREG1 by 1

D7T5:  
 OutBSel: (IR6,IR5); Send SRCREG1 to B input of ALU  
 FunSelALU: 0001; Print SRCREG1 to outALU  
 MuxBSel: 11; Send outALU to ARF input  
 RegSelARF: decode(IR9,IR8); Enable DESTREG  
 FunSelARF: 01; Load result to DESTREG

D7T6:  
 RegSelRF: decode(IR6,IR6); Enable SRCREG1  
 FunSelRF: 10; Increment SRCREG1 back to its original value

OutCSel: (IR9,IR8); Send DESTREG to MuxA  
MuxASel: 10; Send DESTREG to MuxC  
MuxCSel: 0; Send DESTREG to A input of ALU  
FunSelALU: 0000; print DESTREG to outALU

D7T4: IR10IR7: IR9IR8 = IR6IR5:  $ARF \leftarrow ARF - 1$   
RegSelARF: decode(IR6,IR5); Enable SRCREG1  
FunSelARF: 11; Decrement SRCREG1 by 1

D7T5:  
OutCSel: (IR6,IR5); Send SRCREG1/DESTREG to MuxA  
MuxASel: 10; Send SRCREG1/DESTREG to MuxCSel  
MuxCSel: 0; Send SRCREG1/DESTREG to input of A of ALU  
FunSelALU: 0000; Print SRCREG1/DESTREG to outALU

D7T4: IR10IR7: IR9IR8 != IR6IR5:  $ARF \leftarrow ARF - 1$   
RegSelARF: decode(IR6,IR5); Enable SRCREG1  
FunSelARF: 11; Decrement SRCREG1 by 1

D7T5:  
OutCSel: (IR6,IR5); Send SRCREG1 (decremented) to MuxA  
MuxASel: 10; Send SRCREG1 to MuxC  
MuxCSel: 0; Send SRCREG1 to A input of ALU  
FunSelALU: 0000; Print SRCREG1 as outALU  
MuxBSel: 11; Send SRCREG1 to ARF input  
RegSelARF: decode(IR9,IR8); Enable DESTREG  
FunSelARF: 01; Load to DESTREG

D7T6:  
RegSelARF: decode(IR6,IR5); Enable SRCREG1  
FunSelARF: 10; Increment SRCREG1 back to its original value  
OutCSel: (IR9,IR8); Send DESTREG to MuxA  
MuxASel: 10; Send DESTREG to MuxCSel  
MuxCSel: 0; Send DESTREG to A input of ALU  
FunSelALU: 0000; Print DESTREG as outALU

### **2.2.9 INC**

$DESTREG \leftarrow SRCREG1 + 1$

D8T4: IR10'IR7': IR9IR8 = IR6IR5: RF  $\leftarrow$  RF + 1

RegSelRF: decode(IR6,IR5); Enable SRCREG1

FunSelRF: 10; Increment SRCREG1 by 1

D8T5: Fixing flag

OutBSel: (IR6,IR5); Send SRCREG1 to B input of ALU

FunSelALU: 0001; Send B as outALU

D8T4: IR10'IR7': IR9IR8 != IR6IR5: RF  $\leftarrow$  RF + 1

RegSelRF: decode(IR6,IR5); Enable SRCREG1

FunSelRF: 10; Increment SRCREG1 by 1

D8T5:

OutBSel: (IR6,IR5); Send SRCREG1 (incremented) to B input of ALU

FunSelALU: 0001; Print outALU as SRCREG1 (incremented)

MuxASel: 11;

RegSelRF: decode(IR9,IR8); Enable DESTREG

FunSelRF: 01; Load result to DESTREG

D8T6:

OutBSel: (IR9,IR8); Send DESTREG to ALU B input

FunSelALU: 0001; Print outALU as SRCREG1

RegSelRF: decode(IR6,IR5); Enable SRCREG1

FunSelRF: 11; Decrement SRCREG1 back to its original value

D8T4: IR10'IR7': RF  $\leftarrow$  ARF + 1

RegSelARF: decode(IR6,IR5); Enable SRCREG1

FunSelARF: 10; Increment SRCREG1 by 1

D8T5:

OutCSel: (IR6,IR5); Send SRCREG1 (incremented) to MuxA

MuxASel: 10; Send SRCREG1 to RF input

RegSelRF: decode(IR9,IR8); Enable DESTREG

FunSelRF: 01; Load to DESTREG

D8T6:

OutBSel: (IR9,IR8); Send DESTREG to B input of ALU

FunSelALU: 0001; Print outALU as DESTREG

RegSelARF: decode(IR6,IR5); Enable SRCREG1

FunSelARF: 11; Decrement SRCREG1 back to its original value

D8T4: IR10IR7':  $ARF \leftarrow RF + 1$

RegSelRF: decode(IR6,IR5); Enable SRCREG1

FunSelRF: 10; Increment SRCREG1 by 1

D8T5:

OutBSel: (IR6,IR5); Send SRCREG1 to B input of ALU

FunSelALU: 0001; Print SRCREG1 to outALU

MuxBSel: 11; Send outALU to ARF input

RegSelARF: decode(IR9,IR8); Enable DESTREG

FunSelARF: 01; Load result to DESTREG

D8T6:

RegSelRF: decode(IR6,IR6); Enable SRCREG1

FunSelRF: 11; Decrement SRCREG1 back to its original value

OutCSel: (IR9,IR8); Send DESTREG to MuxA

MuxASel: 10; Send DESTREG to MuxC

MuxCSel: 0; Send DESTREG to A input of ALU

FunSelALU: 0000; print DESTREG to outALU

D8T4: IR10IR7: IR9IR8 = IR6IR5:  $ARF \leftarrow ARF + 1$

RegSelARF: decode(IR6,IR5); Enable SRCREG1

FunSelARF: 10; Increment SRCREG1 by 1

D8T5:

OutCSel: (IR6,IR5); Send SRCREG1/DESTREG to MuxA

MuxASel: 10; Send SRCREG1/DESTREG to MuxCSel

MuxCSel: 0; Send SRCREG1/DESTREG to input of A of ALU

FunSelALU: 0000; Print SRCREG1/DESTREG to outALU

D8T4: IR10IR7: IR9IR8 != IR6IR5:  $ARF \leftarrow ARF + 1$

RegSelARF: decode(IR6,IR5); Enable SRCREG1

FunSelARF: 10; Increment SRCREG1 by 1

D8T5:

OutCSel: (IR6,IR5); Send SRCREG1 (incremented) to MuxA

MuxASel: 10; Send SRCREG1 to MuxC



MuxCSel: 0; Send SRCREG1 to A input of ALU  
 FunSelALU: 0000; Print SRCREG1 as outALU  
 MuxBSel: 11; Send SRCREG1 to ARF input  
 RegSelARF: decode(IR9,IR8); Enable DESTREG  
 FunSelARF: 01; Load to DESTREG

D8T6:

RegSelARF: decode(IR6,IR5); Enable SRCREG1  
 FunSelARF: 11; Decrement SRCREG1 back to its original value  
 OutCSel: (IR9,IR8); Send DESTREG to MuxA  
 MuxASel: 10; Send DESTREG to MuxCSel  
 MuxCSel: 0; Send DESTREG to A input of ALU  
 FunSelALU: 0000; Print DESTREG as outALU

## 2.2.10 AND

$\text{DESTREG} \leftarrow \text{SRCREG1 AND SRCREG2}$

D9T4: IR10'IR7'IR4':  $\text{RF} \leftarrow \text{RF AND RF}$   
 OutASel: (IR6,IR5); Send SRCREG1 to MuxC  
 MuxCSel: 1; Send SRCREG1 as A input of ALU  
 OutBSel: (IR3,IR2); Send SRCREG2 as B input of ALU  
 FunSelALU: 0111; Do the operation A AND B  
 MuxASel: 11; Send outALU to RF input  
 RegSelRF: decode(IR9,IR8); Enable DESTREG  
 FunSelRF: 01; Load result to DESTREG

D9T4: IR10'IR7'IR4:  $\text{RF} \leftarrow \text{RF AND ARF}$   
 LEFT FOR LATER (NEED PSH/PUL)

D9T4: IR10'IR7IR4':  $\text{RF} \leftarrow \text{ARF AND RF}$   
 LEFT FOR LATER (NEED PSH/PUL)

D9T4: IR10'IR7IR4:  $\text{RF} \leftarrow \text{ARF AND ARF}$   
 REDUNDANT

D9T4: IR10IR7'IR4':  $\text{ARF} \leftarrow \text{RF AND RF}$   
 OutASel: (IR6,IR5); Send SRCREG1 to MuxC

MuxCSel: 1; Send SRCREG1 to A input of ALU  
 OutBSel: (IR3,IR2); Send SRCREG2 to B input of ALU  
 FunSelALU: 0111; Do the operation A AND B  
 MuxBSel: 11; Send outALU to ARF input  
 RegSelARF: decode(IR9,IR8); Enable DESTREG  
 FunSelARF: 01; Load result to DESTREG

D9T4: IR10IR7'IR4:  $ARF \leftarrow RF \text{ AND } ARF$   
 OutCSel: (IR3,IR2); Send SRCREG2 to MuxA  
 MuxASel: 10; Send SRCREG2 to MuxC  
 MuxCSel: 0; Send SRCREG2 as A input of ALU  
 OutBSel: (IR6,IR5); Send SRCREG1 as B input of ALU  
 FunSelALU; 0111; Do the operation A AND B  
 MuxBSel: 11; Send outALU to ARF input  
 RegSelARF: decode(IR9,IR8); Enable DESTREG  
 FunSelARF: 01; Load result to DESTREG

D9T4: IR10IR7IR4':  $ARF \leftarrow ARF \text{ AND } RF$   
 SAME AS ABOVE ( IR10IR7'IR4:  $ARF \leftarrow RF \text{ AND } ARF$  )

D9T4: IR10IR7IR4:  $ARF \leftarrow ARF \text{ AND } ARF$   
 REDUNDANT

### 2.2.11 OR

$DESTREG \leftarrow SRCREG1 \text{ OR } SRCREG2$

D10T4: IR10'IR7'IR4':  $RF \leftarrow RF \text{ OR } RF$   
 OutASel: (IR6,IR5); Send SRCREG1 to MuxC  
 MuxCSel: 1; Send SRCREG1 as A input of ALU  
 OutBSel: (IR3,IR2); Send SRCREG2 as B input of ALU  
 FunSelALU: 1000; Do the operation A AND B  
 MuxASel: 11; Send outALU to RF input  
 RegSelRF: decode(IR9,IR8); Enable DESTREG  
 FunSelRF: 01; Load result to DESTREG

D10T4: IR10'IR7'IR4:  $RF \leftarrow RF \text{ OR } ARF$   
 LEFT FOR LATER (NEED PSH/PUL)

D10T4: IR10'IR7IR4':  $RF \leftarrow ARF \text{ OR } RF$   
LEFT FOR LATER (NEED PSH/PUL)

D10T4: IR10'IR7IR4:  $RF \leftarrow ARF \text{ OR } ARF$   
REDUNDANT

D10T4: IR10IR7'IR4':  $ARF \leftarrow RF \text{ OR } RF$   
OutASel: (IR6,IR5); Send SRCREG1 to MuxC  
MuxCSel: 1; Send SRCREG1 to A input of ALU  
OutBSel: (IR3,IR2); Send SRCREG2 to B input of ALU  
FunSelALU: 1000; Do the operation A AND B  
MuxBSel: 11; Send outALU to ARF input  
RegSelARF: decode(IR9,IR8); Enable DESTREG  
FunSelARF: 01; Load result to DESTREG

D10T4: IR10IR7'IR4:  $ARF \leftarrow RF \text{ OR } ARF$   
OutCSel: (IR3,IR2); Send SRCREG2 to MuxA  
MuxASel: 10; Send SRCREG2 to MuxC  
MuxCSel: 0; Send SRCREG2 as A input of ALU  
OutBSel: (IR6,IR5); Send SRCREG1 as B input of ALU  
FunSelALU; 1000; Do the operation A AND B  
MuxBSel: 11; Send outALU to ARF input  
RegSelARF: decode(IR9,IR8); Enable DESTREG  
FunSelARF: 01; Load result to DESTREG

D10T4: IR10IR7IR4':  $ARF \leftarrow ARF \text{ OR } RF$   
SAME AS ABOVE ( IR10IR7'IR4:  $ARF \leftarrow RF \text{ AND } ARF$  )

D10T4: IR10IR7IR4:  $ARF \leftarrow ARF \text{ OR } ARF$   
REDUNDANT

### **2.2.12 NOT**

$DESTREG \leftarrow \text{NOT SRCREG1}$

D11T4: IR10'IR7' :  $RF \leftarrow RF$   
OutBSel: (IR6,IR5); Send SRCREG1 as B input of ALU  
FunSelALU; 0011; Do the operation -B

MuxASel: 11; Send outALU to RF input  
RegSelRF: decode(IR9,IR8); Enable DESTREG  
FunSelRF: 01; Load result to DESTREG

D11T4: IR10'IR7 : RF  $\leftarrow$  ARF  
LEFT FOR LATER (NEED PSH/PUL)

D11T4: IR10IR7 : ARF  $\leftarrow$  ARF  
OutCSel: (IR6,IR5); Select SRCREG1 to MuxA  
MuxASel: 10; Send SRCREG1 to MuxC  
MuxCSel: 0; Send SRCREG1 as A input of ALU  
FunSelALU: 0010; Do the operation -A  
MuxBSel: 11; Send outALU to input of ARF  
RegSelARF: decode(IR9,IR8); Enable DESTREG  
FunSelARF: 01; Load result to DESTREG

D11T4: IR10IR7' : ARF  $\leftarrow$  RF  
OutBSel: (IR6,IR5); Send SRCREG1 as B input of ALU  
FunSelALU; 0011; Do the operation -B  
MuxBSel: 11; Send outALU to input of ARF  
RegSelARF: decode(IR9,IR8); Enable DESTREG  
FunSelARF: 01; Load result to DESTREG

### **2.2.13 LSL**

DESTREG  $\leftarrow$  LSL SRCREG1

D12T4: IR10'IR7' : RF  $\leftarrow$  RF  
OutASel: (IR6,IR5); Send SRCREG1 as A input of ALU  
MuxCSel: 1; Send SRCREG1 as A input of ALU  
FunSelALU; 1010 ; Do the operation LSL  
MuxASel: 11; Send outALU to RF input  
RegSelRF: decode(IR9,IR8); Enable DESTREG  
FunSelRF: 01; Load result to DESTREG

D12T4: IR10'IR7 : RF  $\leftarrow$  ARF  
LEFT FOR LATER (NEED PSH/PUL)

D12T4: IR10IR7 :  $ARF \leftarrow ARF$   
 OutCSel: (IR6,IR5); Select SRCREG1 to MuxA  
 MuxASel: 10; Send SRCREG1 to MuxC  
 MuxCSel: 0; Send SRCREG1 as A input of ALU  
 FunSelALU; 1010 ; Do the operation LSL  
 MuxBSel: 11; Send outALU to input of ARF  
 RegSelARF: decode(IR9,IR8); Enable DESTREG  
 FunSelARF: 01; Load result to DESTREG

D12T4: IR10IR7' :  $ARF \leftarrow RF$   
 OutASel: (IR6,IR5); Send SRCREG1 as A input of ALU  
 MuxCSel: 0; Send SRCREG1 as A input of ALU  
 FunSelALU; 1010 ; Do the operation LSL  
 MuxBSel: 11; Send outALU to input of ARF  
 RegSelARF: decode(IR9,IR8); Enable DESTREG  
 FunSelARF: 01; Load result to DESTREG

#### 2.2.14 LSR

$DESTREG \leftarrow LSR SRCREG1$

D13T4: IR10'IR7' :  $RF \leftarrow RF$   
 OutASel: (IR6,IR5); Send SRCREG1 as A input of ALU  
 MuxCSel: 0; Send SRCREG1 as A input of ALU  
 FunSelALU; 1011 ; Do the operation LSL  
 MuxASel: 11; Send outALU to RF input  
 RegSelRF: decode(IR9,IR8); Enable DESTREG  
 FunSelRF: 01; Load result to DESTREG

D13T4: IR10'IR7 :  $RF \leftarrow ARF$   
 LEFT FOR LATER (NEED PSH/PUL)

D13T4: IR10IR7 :  $ARF \leftarrow ARF$   
 OutCSel: (IR6,IR5); Select SRCREG1 to MuxA  
 MuxASel: 10; Send SRCREG1 to MuxC  
 MuxCSel: 0; Send SRCREG1 as A input of ALU  
 FunSelALU; 1011 ; Do the operation LSL  
 MuxBSel: 11; Send outALU to input of ARF

RegSelARF: decode(IR9,IR8); Enable DESTREG

FunSelARF: 01; Load result to DESTREG

D13T4: IR10IR7' :  $ARF \leftarrow RF$

OutASel: (IR6,IR5); Send SRCREG1 as A input of ALU

MuxCSel: 0; Send SRCREG1 as A input of ALU

FunSelALU; 1011 ; Do the operation LSL

MuxBSel: 11; Send outALU to input of ARF

RegSelARF: decode(IR9,IR8); Enable DESTREG

FunSelARF: 01; Load result to DESTREG

### **2.2.15 BRA**

$PC \leftarrow \text{Value}$

Addressing Mode is Immediate, So,

$PC \leftarrow IR(7-0)$

D14T4:

MuxBSel: 01; Send IR(7-0) to ARF input

RegSelARF: 001; Enable PC

FunSelARF: 01; Load IR(7-0) to PC

### **2.2.16 BEQ**

IF Z=1 THEN  $PC \leftarrow \text{Value}$

Addressing Mode is Immediate, So,

IF Z=1 THEN  $PC \leftarrow IR(7-0)$

D15T4: Z': DO NOTHING

D15T4: Z:

MuxBSel: 01; Send IR(7-0) to ARF input

RegSelARF: 001; Enable PC

FunSelARF: 01; Load IR(7-0) to PC

### **2.2.17 BNE**

IF Z=0 THEN  $PC \leftarrow \text{Value}$

Addressing Mode is Immediate, So,

IF Z=0 THEN  $PC \leftarrow IR(7-0)$

D16T4: Z': DO NOTHING

D16T4: Z':

MuxBSel: 01; Send IR(7-0) to ARF input

RegSelARF: 001; Enable PC

FunSelARF: 01; Load IR(7-0) to PC

### **2.2.18 CALL**

$M[SP] \leftarrow PC$ ,  $SP \leftarrow SP - 1$ ,  $PC \leftarrow \text{Value}$

Addressing Mode is Immediate, So,

$M[SP] \leftarrow PC$ ,  $SP \leftarrow SP - 1$ ,  $PC \leftarrow IR(7-0)$

D17T4:

OutCSel: 00; Send PC to MuxA

MuxASel: 10; Send PC to MuxC

MuxCSel: 0; Send PC as input A of ALU

FunSelALU: 0000; Select PC as output of ALU

OutDSel: 10; Send SP to address of M

Store: 1;

D17T5:

RegSelARF: 100; Enable SP

FunSelARF: 11; Decrement SP by 1

D17T6:

MuxBSel: 01; Send IR(7-0) to ARF input

RegSelARF: 001; Enable PC

FunSelARF: 01; Load IR(7-0) to PC

### **2.2.19 RET**

$SP \leftarrow SP + 1$ ,  $PC \leftarrow M[SP]$

D18T4:

RegSelARF: 100; Enable SP

FunSelARF: 10; Increment SP by 1

D18T5:

OutDSel: 10; Select SP as the address of M

Load: 1; Load M[SP]  
MuxBSel: 10; Send M[SP] to ARF input  
RegSelARF: 001; Enable PC  
FunSelARF: 01; Load M[SP] to PC

## 3 PROJECT EQUATIONS

### 3.1 ORIGINAL

We firstly implemented our circuit without the INC and DEC operations

#### 3.1.1 OutASel

D1T5: IR10, IR9;  
D2T4: IR10'IR7': (IR6,IR5);  
D2T4: IR10IR7': (IR6,IR5)  
D3T4: (IR10,IR9)  
D5T4: IR10'IR7'IR4': (IR6,IR5)  
D5T4: IR10IR7'IR4': (IR6,IR5)  
D6T4: IR10'IR4'IR7': (IR3,IR2)  
D6T4: IR10IR4'IR7': (IR3,IR2);  
D9T4: IR10'IR7'IR4': (IR6,IR5);  
D9T4: IR10IR7'IR4': (IR6,IR5);  
D10T4: IR10'IR7'IR4': (IR6,IR5);  
D10T4: IR10IR7'IR4': (IR6,IR5)  
D12T4: IR10'IR7': (IR6,IR5)  
D12T4: IR10IR7': (IR6,IR5)  
D13T4: IR10'IR7' : (IR6,IR5);  
D13T4: IR10IR7': (IR6,IR5);

#### 3.1.2 OutBSel

D5T4: IR10'IR7'IR4': (IR3,IR2);  
D5T4: IR10IR7'IR4': (IR3,IR2)  
D5T4: IR10IR7'IR4: (IR6,IR5)  
D5T4: IR10IR7IR4': (IR3,IR2)  
D6T4: IR10'IR4'IR7': (IR6,IR5)  
D6T4: IR10'IR4IR7': (IR6,IR5)  
D6T4: IR10IR4'IR7': (IR6,IR5);



D6T4: IR10IR4IR7': (IR6,IR5);  
 D9T4: IR10'IR7'IR4': (IR3,IR2);  
 D9T4: IR10IR7'IR4': (IR3,IR2);  
 D9T4: IR10IR7'IR4: (IR6,IR5);  
 D9T4: IR10IR7IR4': (IR6,IR5);  
 D10T4: IR10'IR7'IR4': (IR3,IR2);  
 D10T4: IR10IR7'IR4': (IR3,IR2);  
 D10T4: IR10IR7'IR4: (IR6,IR5);  
 D10T4: IR10IR7IR4': (IR6,IR5);  
 D11T4: IR10'IR7' : (IR6,IR5);  
 D11T4: IR10IR7': (IR6,IR5);

### 3.1.3 RegSelRF

D0T4: IR(8) = 0, decode(IR10,IR9);  
 D0T5: IR(8) = 1, decode(IR10,IR9)  
 D2T4: IR10'IR7': decode(IR9,IR8)  
 D2T4: IR10'IR7: decode(IR9,IR8)  
 D4T5: decode(IR10,IR9)  
 D5T4: IR10'IR7'IR4': decode(IR9,IR8)  
 D6T4: IR10'IR4'IR7': decode(IR9,IR8);  
 D6T5: IR10'IR4IR7': decode(IR9,IR8);  
 D9T4: IR10'IR7'IR4': decode(IR9,IR8)  
 D10T4: IR10'IR7'IR4': decode(IR9,IR8);  
 D11T4: IR10'IR7' : decode(IR9,IR8)  
 D12T4: IR10'IR7' : decode(IR9,IR8);  
 D13T4: IR10'IR7' : decode(IR9,IR8);

### 3.1.4 FunSelRF

D0T4: IR(8) = 0, 01;  
 D0T5: 01;  
 D2T4: IR10'IR7': 01;  
 D2T4: IR10'IR7: 01;  
 D4T5: 01;  
 D5T4: IR10'IR7'IR4': 01;  
 D6T4: IR10'IR4'IR7': 01;  
 D6T5: IR10'IR4IR7': 01  
 D9T4: IR10'IR7'IR4': 01;

D10T4: IR10'IR7'IR4': 01;  
 D11T4: IR10'IR7' : 01;  
 D12T4: IR10'IR7' : 01;  
 D13T4: IR10'IR7' : 01;

### 3.1.5 MuxCSel

D1T5: 1  
 D2T4: IR10IR7': 1  
 D2T4: IR10IR7: 0;  
 D3T4: 1;  
 D5T4: IR10'IR7'IR4': 1;  
 D5T4: IR10IR7'IR4': 1;  
 D5T4: IR10IR7'IR4: 0;  
 D5T4: IR10IR7IR4': 0;  
 D6T4: IR10'IR4'IR7': 1;  
 D6T4: IR10'IR4IR7': 0;  
 D6T4: IR10IR4'IR7': 1;  
 D6T4: IR10IR4IR7': 0;  
 D9T4: IR10'IR7'IR4': 1;  
 D9T4: IR10IR7'IR4': 1;  
 D9T4: IR10IR7'IR4: 0;  
 D9T4: IR10IR7IR4': 0;  
 D10T4: IR10'IR7'IR4': 1;  
 D10T4: IR10IR7'IR4': 1;  
 D10T4: IR10IR7'IR4: 0;  
 D10T4: IR10IR7IR4': 0;  
 D11T4: IR10IR7 : 0;  
 D12T4: IR10'IR7' : 1;  
 D12T4: IR10IR7 : 0;  
 D12T4: IR10IR7' : 0;  
 D13T4: IR10'IR7' : 0;  
 D13T4: IR10IR7 : 0;  
 D13T4: IR10IR7' : 0;  
 D17T4: 0;

### 3.1.6 FunSelALU

D1T5: 0000;

D2T4: IR10'IR7': 0000;  
D2T4: IR10IR7': 0000;  
D2T4: IR10IR7: 0000;  
D3T4: 0000;  
D5T4: IR10'IR7'IR4': 0100;  
D5T4: IR10IR7'IR4': 0100;  
D5T4: IR10IR7'IR4: 0100;  
D5T4: IR10IR7IR4': 0100;  
D6T4: IR10'IR4'IR7': 0110;  
D6T5: IR10'IR4IR7': 0110;  
D6T4: IR10IR4'IR7': 0110;  
D6T4: IR10IR4IR7': 0110;  
D9T4: IR10'IR7'IR4': 0111;  
D9T4: IR10IR7'IR4': 0111;  
D9T4: IR10IR7'IR4: 0111;  
D9T4: IR10IR7IR4': 0111;  
D10T4: IR10'IR7'IR4': 1000;  
D10T4: IR10IR7'IR4': 1000;  
D10T4: IR10IR7'IR4: 1000;  
D10T4: IR10IR7IR4': 1000;  
D11T4: IR10'IR7' : 0011;  
D11T4: IR10IR7 : 0010;  
D11T4: IR10IR7' : 0011;  
D12T4: IR10'IR7' : 1010;  
D12T4: IR10IR7 : 1010;  
D12T4: IR10IR7' : 1010;  
D13T4: IR10'IR7' : 1011;  
D13T4: IR10IR7 : 1011;  
D13T4: IR10IR7' : 1011;  
D17T4: 0000;

### 3.1.7 MuxASel

IR(8) = 0, D0T4: 00;  
IR(8) = 1, D0T5: 01;  
D2T4: IR10'IR7': 11;  
D2T4: IR10'IR7: 10;  
D2T4: IR10IR7: 10;

D4T5: 01;  
D5T4: IR10'IR7'IR4': 11;  
D5T4: IR10IR7'IR4: 10;  
D5T4: IR10IR7IR4': 10;  
D6T4: IR10'IR4'IR7': 11;  
D6T4: IR10'IR4IR7': 10;  
D6T5: IR10'IR4IR7': 11;  
D6T4: IR10IR4IR7': 10;  
D9T4: IR10'IR7'IR4': 11;  
D9T4: IR10IR7'IR4: 10;  
D9T4: IR10IR7IR4': 10;  
D10T4: IR10'IR7'IR4': 11;  
D10T4: IR10IR7'IR4: 10;  
D10T4: IR10IR7IR4': 10;  
D11T4: IR10'IR7' : 11;  
D11T4: IR10IR7 : 10;  
D12T4: IR10'IR7' : 11;  
D12T4: IR10IR7 : 10;  
D13T4: IR10'IR7' : 11;  
D13T4: IR10IR7 : 10;  
D17T4: 10;

### 3.1.8 En

T0: 1;  
T1: 0;  
T2: 1;  
T3: 0;

### 3.1.9 L/H

T0: 1;  
T2: 0;

### 3.1.10 FunSelIR

T0: 11;  
T2: 11;

### 3.1.11 MuxBSel

D0T4:  $\text{IR}(8) = 1, 01;$   
D1T4: 01;  
D2T4:  $\text{IR}_{10}\text{IR}_{7'}: 11;$   
D2T4:  $\text{IR}_{10}\text{IR}_7: 11;$   
D5T4:  $\text{IR}_{10}\text{IR}_{7'}\text{IR}_{4'}: 11;$   
D5T4:  $\text{IR}_{10}\text{IR}_{7'}\text{IR}_4: 11;$   
D5T4:  $\text{IR}_{10}\text{IR}_7\text{IR}_{4'}: 11;$   
D6T4:  $\text{IR}_{10}\text{IR}_{4'}\text{IR}_{7'}: 11;$   
D6T4:  $\text{IR}_{10}\text{IR}_4\text{IR}_{7'}: 11;$   
D9T4:  $\text{IR}_{10}\text{IR}_{7'}\text{IR}_{4'}: 11;$   
D9T4:  $\text{IR}_{10}\text{IR}_{7'}\text{IR}_4: 11;$   
D9T4:  $\text{IR}_{10}\text{IR}_7\text{IR}_{4'}: 11;$   
D10T4:  $\text{IR}_{10}\text{IR}_{7'}\text{IR}_{4'}: 11;$   
D10T4:  $\text{IR}_{10}\text{IR}_{7'}\text{IR}_4: 11;$   
D10T4:  $\text{IR}_{10}\text{IR}_7\text{IR}_{4'}: 11;$   
D11T4:  $\text{IR}_{10}\text{IR}_7: 11;$   
D11T4:  $\text{IR}_{10}\text{IR}_{7'}: 11;$   
D12T4:  $\text{IR}_{10}\text{IR}_7: 11;$   
D12T4:  $\text{IR}_{10}\text{IR}_{7'}: 11;$   
D13T4:  $\text{IR}_{10}\text{IR}_7: 11;$   
D13T4:  $\text{IR}_{10}\text{IR}_{7'}: 11;$   
D14T4: 01;  
D15T4: Z: 01  
D16T4:  $Z': 01;$   
D17T6: 01;  
D18T5: 10;

### 3.1.12 Store

D1T5: 1;  
D3T4: 1;  
D17T4: 1;

### 3.1.13 Load

T0: 1;  
T2: 1;

D0T5: 1;  
D4T5: 1;  
D18T5: 1;

### 3.1.14 FunSelARF

T1: 10;  
T3: 10;  
D0T4:  $\text{IR}(8) = 1, 01$ ;  
D1T4: 01;  
D2T4:  $\text{IR}_{10}\text{IR}_{7'}: 01$ ;  
D2T4:  $\text{IR}_{10}\text{IR}_7: 01$ ;  
D3T5: 11;  
D4T4: 10;  
D5T4:  $\text{IR}_{10}\text{IR}_{7'}\text{IR}_{4'}: 01$ ;  
D5T4:  $\text{IR}_{10}\text{IR}_{7'}\text{IR}_4: 01$ ;  
D5T4:  $\text{IR}_{10}\text{IR}_7\text{IR}_{4'}: 01$ ;  
D6T4:  $\text{IR}_{10}\text{IR}_{4'}\text{IR}_{7'}: 01$ ;  
D6T4:  $\text{IR}_{10}\text{IR}_4\text{IR}_{7'}: 01$ ;  
D9T4:  $\text{IR}_{10}\text{IR}_{7'}\text{IR}_{4'}: 01$ ;  
D9T4:  $\text{IR}_{10}\text{IR}_{7'}\text{IR}_4: 01$ ;  
D9T4:  $\text{IR}_{10}\text{IR}_7\text{IR}_{4'}: 01$ ;  
D10T4:  $\text{IR}_{10}\text{IR}_{7'}\text{IR}_{4'}: 01$ ;  
D10T4:  $\text{IR}_{10}\text{IR}_{7'}\text{IR}_4: 01$ ;  
D10T4:  $\text{IR}_{10}\text{IR}_7\text{IR}_{4'}: 01$ ;  
D11T4:  $\text{IR}_{10}\text{IR}_7 : 01$ ;  
D11T4:  $\text{IR}_{10}\text{IR}_{7'} : 01$ ;  
D12T4:  $\text{IR}_{10}\text{IR}_7 : 01$ ;  
D12T4:  $\text{IR}_{10}\text{IR}_{7'} : 01$ ;  
D13T4:  $\text{IR}_{10}\text{IR}_7 : 01$ ;  
D13T4:  $\text{IR}_{10}\text{IR}_{7'} : 01$ ;  
D14T4: 01;  
D15T4: Z: 01;  
D16T4:  $Z': 01$ ;  
D17T5: 11; 01;  
D17T6: 01; 01;  
D18T4: 10; 01;  
D18T5: 01; 01;

### 3.1.15 RegSelARF

T1: 001;  
T3: 001;  
D0T4:  $IR(8) = 1, 010$ ;  
D1T4: 010;  
D2T4:  $IR_{10}IR_{7'}: \text{decode}(IR_9, IR_8)$ ;  
D2T4:  $IR_{10}IR_7: \text{decode}(IR_9, IR_8)$ ;  
D3T5: 100;  
D4T4: 100;  
D5T4:  $IR_{10}IR_{7'}IR_{4'}: \text{decode}(IR_9, IR_8)$ ;  
D5T4:  $IR_{10}IR_{7'}IR_4: \text{decode}(IR_9, IR_8)$ ;  
D5T4:  $IR_{10}IR_7IR_{4'}: \text{decode}(IR_9, IR_8)$ ;  
D6T4:  $IR_{10}IR_{4'}IR_{7'}: \text{decode}(IR_9, IR_8)$ ;  
D6T4:  $IR_{10}IR_4IR_{7'}: \text{decode}(IR_9, IR_8)$ ;  
D9T4:  $IR_{10}IR_{7'}IR_{4'}: \text{decode}(IR_9, IR_8)$ ;  
D9T4:  $IR_{10}IR_{7'}IR_4: \text{decode}(IR_9, IR_8)$ ;  
D9T4:  $IR_{10}IR_7IR_{4'}: \text{decode}(IR_9, IR_8)$ ;  
D10T4:  $IR_{10}IR_{7'}IR_{4'}: \text{decode}(IR_9, IR_8)$ ;  
D10T4:  $IR_{10}IR_{7'}IR_4: \text{decode}(IR_9, IR_8)$ ;  
D10T4:  $IR_{10}IR_7IR_{4'}: \text{decode}(IR_9, IR_8)$ ;  
D11T4:  $IR_{10}IR_7 : \text{decode}(IR_9, IR_8)$ ;  
D11T4:  $IR_{10}IR_{7'} : \text{decode}(IR_9, IR_8)$ ;  
D12T4:  $IR_{10}IR_7 : \text{decode}(IR_9, IR_8)$ ;  
D12T4:  $IR_{10}IR_{7'} : \text{decode}(IR_9, IR_8)$ ;  
D13T4:  $IR_{10}IR_7 : \text{decode}(IR_9, IR_8)$ ;  
D13T4:  $IR_{10}IR_{7'} : \text{decode}(IR_9, IR_8)$ ;  
D14T4: 001;  
D15T4: Z: 001;  
D16T4:  $Z': 001$ ;  
D17T5: 100;  
D17T6: 001;  
D18T4: 100;  
D18T5: 001;

### 3.1.16 OutCSel

D2T4:  $IR_{10}'IR_7: (IR_6, IR_5)$ ;

D2T4: IR10IR7: (IR6,IR5);  
 D5T4: IR10IR7'IR4: (IR3,IR2);  
 D5T4: IR10IR7IR4': (IR6,IR5);  
 D6T4: IR10'IR4IR7': (IR3,IR2);  
 D6T4: IR10IR4IR7': (IR3,IR2);  
 D9T4: IR10IR7'IR4: (IR3,IR2);  
 D9T4: IR10IR7IR4': (IR3,IR2);  
 D10T4: IR10IR7'IR4: (IR3,IR2);  
 D10T4: IR10IR7IR4': (IR3,IR2);  
 D11T4: IR10IR7 : (IR6,IR5);  
 D12T4: IR10IR7 : (IR6,IR5);  
 D13T4: IR10IR7 : (IR6,IR5);  
 D17T4: 00;

### 3.1.17 OutDSel

T0: 00;  
 T1: 00;  
 T2: 00;  
 T3: 00;  
 D0T5: 01;  
 D1T5: 01;  
 D3T4: 10;  
 D4T5: 10;  
 D17T4: 10;  
 D18T5: 10;

### 3.1.18 SC Clear

D0T4IR8'  
 D0T5IR8  
 D1T5  
 D2T4  
 D3T5  
 D4T5  
 D5T4  
 D6T4IR10'IR4'IR7'  
 D6T4IR10'IR4'IR7  
 D6T5IR10'IR4IR7'



D6T4IR10'IR4IR7  
D6T4IR10IR4'IR7'  
D6T4IR10IR4'IR7  
D6T4IR10IR4IR7'  
D6T4IR10IR4IR7  
D7T5: IR10'IR7': SRC==DEST  
D7T5: IR10'IR7': !(SRC==DEST)  
D7T6: IR10'IR7  
D7T6: IR10IR7'  
D7T5: IR10IR7: SRC==DEST  
D7T6: IR10IR7: !(SRC==DEST)  
D8T5: IR10'IR7': SRC==DEST  
D8T5: IR10'IR7': !(SRC==DEST)  
D8T6: IR10'IR7  
D8T6: IR10IR7'  
D8T5: IR10IR7: SRC==DEST  
D8T6: IR10IR7: !(SRC==DEST)  
D9T4  
D10T4  
D11T4  
D12T4  
D13T4  
D14T4  
D15T4  
D16T4  
D17T6  
D18T5

## 3.2 COMPLETE

We managed to find a way to implement INC and DEC operations.

### 3.2.1 RegSelRF

D7T4: IR10'IR7': decode(IR6,IR5);  
D7T5: IR10'IR7': IR9IR8 != IR6IR5: decode(IR9,IR8);  
D7T6: IR10'IR7': IR9IR8 != IR6IR5: decode(IR6,IR5);  
D7T5: IR10'IR7: decode(IR9,IR8);

D7T4: IR10IR7': decode(IR6,IR5);  
 D7T6: IR10IR7': decode(IR6,IR6);  
 D8T4: IR10'IR7': decode(IR6,IR5);  
 D8T5: IR10'IR7': IR9IR8 != IR6IR5: decode(IR9,IR8);  
 D8T6: IR10'IR7': IR9IR8 != IR6IR5: decode(IR6,IR5);  
 D8T5: IR10'IR7: decode(IR9,IR8);  
 D8T4: IR10IR7': decode(IR6,IR5);  
 D8T6: IR10IR7': decode(IR6,IR6);

### 3.2.2 FunSelRF

D7T4: IR10'IR7': 11;  
 D7T5: IR10'IR7': IR9IR8 != IR6IR5: 01;  
 D7T6: IR10'IR7': IR9IR8 != IR6IR5: 10;  
 D7T5: IR10'IR7: 01;  
 D7T4: IR10IR7': 11;  
 D7T6: IR10IR7': 10;  
 D8T4: IR10'IR7': 10;  
 D8T5: IR10'IR7': IR9IR8 != IR6IR5: 01;  
 D8T6: IR10'IR7': IR9IR8 != IR6IR5: 11;  
 D8T5: IR10'IR7: 01;  
 D8T4: IR10IR7': 10;  
 D8T6: IR10IR7': 11;

### 3.2.3 OutBSel

D7T5: IR10'IR7': (IR6,IR5);  
 D7T6: IR10'IR7': IR9IR8 != IR6IR5: (IR9,IR8);  
 D7T6: IR10'IR7: (IR9,IR8);  
 D7T5: IR10IR7': (IR6,IR5);  
 D8T5: IR10'IR7': (IR6,IR5);  
 D8T6: IR10'IR7': IR9IR8 != IR6IR5: (IR9,IR8);  
 D8T6: IR10'IR7: (IR9,IR8);  
 D8T5: IR10IR7': (IR6,IR5);

### 3.2.4 FunSelALU

D7T5: IR10'IR7': 0001;  
 D7T6: IR10'IR7': IR9IR8 != IR6IR5: 0001;

D7T6: IR10'IR7: 0001;  
D7T5: IR10IR7': 0001;  
D7T6: IR10IR7': 0000;  
D7T5: IR10IR7: 0000;  
D7T6: IR10IR7: IR9IR8 != IR6IR5: 0000;  
D8T5: IR10'IR7': 0001;  
D8T6: IR10'IR7': IR9IR8 != IR6IR5: 0001;  
D8T6: IR10'IR7: 0001;  
D8T5: IR10IR7': 0001;  
D8T6: IR10IR7': 0000;  
D8T5: IR10IR7: 0000;  
D8T6: IR10IR7: IR9IR8 != IR6IR5: 0000;

### 3.2.5 MuxASel

D7T5: IR10'IR7': IR9IR8 != IR6IR5: 11;  
D7T5: IR10'IR7: 10;  
D7T6: IR10IR7': 10;  
D7T5: IR10IR7: IR9IR8 = IR6IR5:10;  
D7T5: IR10IR7: IR9IR8 != IR6IR5: 10;  
D7T6: IR10IR7: IR9IR8 != IR6IR5: 10;  
D8T5: IR10'IR7': IR9IR8 != IR6IR5: 11;  
D8T5: IR10'IR7: 10;  
D8T6: IR10IR7': 10;  
D8T5: IR10IR7: IR9IR8 = IR6IR5:10;  
D8T5: IR10IR7: IR9IR8 != IR6IR5: 10;  
D8T6: IR10IR7: IR9IR8 != IR6IR5: 10;

### 3.2.6 FunSelARF

D7T4: IR10'IR7: 11;  
D7T6: IR10'IR7: 10;  
D7T5: IR10IR7': 01;  
D7T4: IR10IR7: 11;  
D7T5: IR10IR7: IR9IR8 != IR6IR5: 01;  
D7T6: IR10IR7: IR9IR8 != IR6IR5: 10;  
D8T4: IR10'IR7: 10;  
D8T6: IR10'IR7: 11;  
D8T5: IR10IR7': 01;

D8T4: IR10IR7: 10;  
D8T5: IR10IR7: IR9IR8 != IR6IR5: 01;  
D8T6: IR10IR7: IR9IR8 != IR6IR5: 11;

### 3.2.7 OutCSel

D7T5: IR10'IR7: (IR6,IR5);  
D7T6: IR10IR7': (IR9,IR8);  
D7T4: IR10IR7: IR9IR8 = IR6IR5: (IR6,IR5);  
D7T5: IR10IR7: IR9IR8 != IR6IR5: (IR6,IR5);  
D7T6: IR10IR7: IR9IR8 != IR6IR5: (IR9,IR8);  
D8T5: IR10'IR7: (IR6,IR5);  
D8T6: IR10IR7': (IR9,IR8);  
D8T4: IR10IR7: IR9IR8 = IR6IR5: (IR6,IR5);  
D8T5: IR10IR7: IR9IR8 != IR6IR5: (IR6,IR5);  
D8T6: IR10IR7: IR9IR8 != IR6IR5: (IR9,IR8);

### 3.2.8 RegSelARF

D7T4: IR10'IR7: decode(IR6,IR5);  
D7T6: IR10'IR7: decode(IR6,IR5);  
D7T5: IR10IR7': decode(IR9,IR8);  
D7T4: IR10IR7: decode(IR6,IR5);  
D7T5: IR10IR7: IR9IR8 != IR6IR5: decode(IR9,IR8);  
D7T6: IR10IR7: IR9IR8 != IR6IR5: decode(IR6,IR5);  
D8T4: IR10'IR7: decode(IR6,IR5);  
D8T6: IR10'IR7: decode(IR6,IR5);  
D8T5: IR10IR7': decode(IR9,IR8);  
D8T4: IR10IR7: decode(IR6,IR5);  
D8T5: IR10IR7: IR9IR8 != IR6IR5: decode(IR9,IR8);  
D8T6: IR10IR7: IR9IR8 != IR6IR5: decode(IR6,IR5);

### 3.2.9 MuxBSel

D7T5: IR10IR7': 11;  
D7T5: IR10IR7: IR9IR8 != IR6IR5: 11;  
D8T5: IR10IR7': 11;  
D8T5: IR10IR7: IR9IR8 != IR6IR5: 11;

### 3.2.10 MuxCSel

D7T6: IR10IR7': 0;

D7T5: IR10IR7: 0;

D7T6: IR10IR7: IR9IR8 != IR6IR5: 0;

D8T6: IR10IR7': 0;

D8T5: IR10IR7: 0;

D8T6: IR10IR7: IR9IR8 != IR6IR5: 0;

## 4 RESULTS

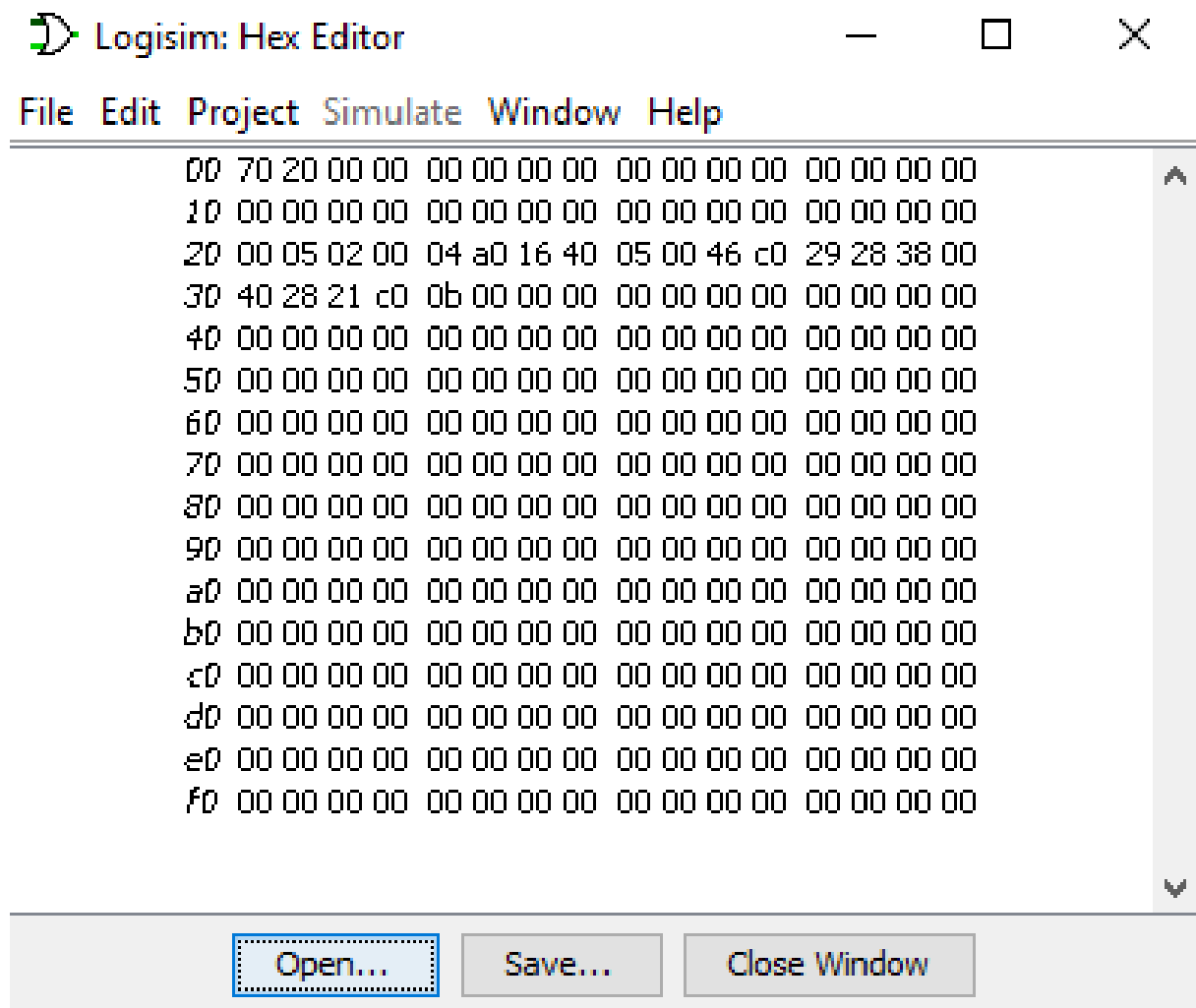


Figure 4: Full Circuit

We tried to test our implementation with the given example, but our circuit did not work properly. It did not stop at the desired T clock signal.

## 5 DISCUSSION

First of all, we designed a way to implement all of the opcodes which are given in pdf file by deciding whenever the selected bits are ‘1’ according to time signals. Secondly, we sorted this list according to input variables. Both of the lists are added to the report.

## 6 CONCLUSION

In this project, we designed a basic computer. The project, this time around, was extremely long and tedious. We couldn’t managed to track the mistakes we made on time. We implemented the circuit to the best of our abilities.

To conclude, this project helped us learn how CPU handles different kinds of instructions.